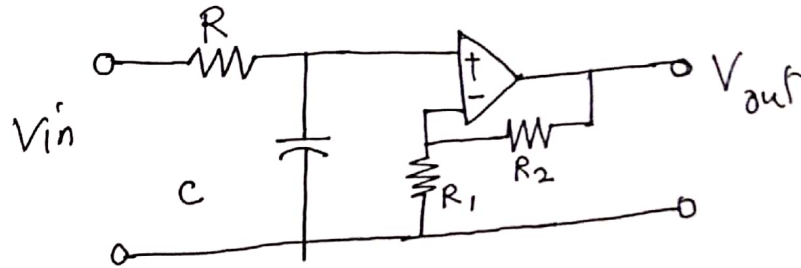


Problem 1 : Design a non-inverting active low pass filter circuit that has a gain of ten at low frequencies and the cut-off frequency is 250 Hz.

Solⁿ: Low pass filter circuit is :



The gain for non-inverting amplifier is given as:

$$A = 1 + \frac{R_2}{R_1} = 10$$

Assume a value for resistor R_1 of $1\text{ k}\Omega$.

$$\text{So, } R_2 = (10 - 1) \times R_1 = 9\text{ k}\Omega.$$

The cut off frequency is given as 250 Hz.

$$\text{So, } \frac{1}{2\pi RC} = 250.$$

Assume a value for R as $10\text{ k}\Omega$


$$\frac{1}{2\pi \times 10 \times 10^3 \times C} = 250$$

$$\text{So, } C = \frac{1}{2 \times 3.1416 \times 10^4 \times 250} = 6.366 \times 10^{-8}\text{ F} = 63.6 \times 10^{-9}\text{ F}$$

$$= 63.6\text{ nF}$$

$$[1\text{ nF} = 10^{-9}\text{ F}]$$

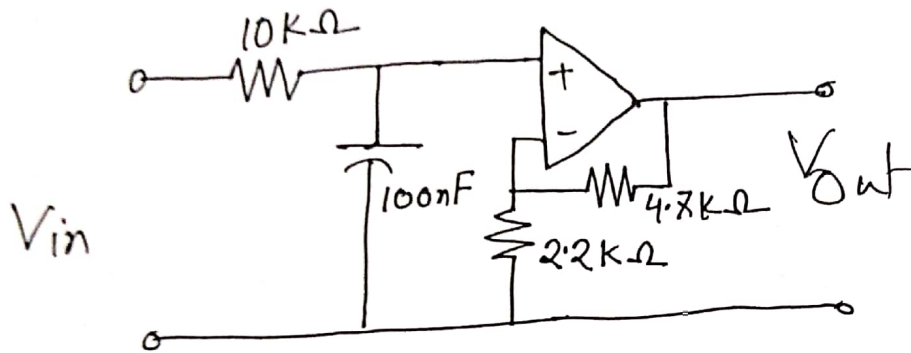Problem 2: Find the cut-off or corner frequency for the following filter circuit:



Solⁿ: We know, the cut-off frequency is:

$$f_c = \frac{1}{2\pi RC}$$

$$= \frac{1}{2 \times 3.1416 \times 10 \times 10^3 \times 100 \times 10^{-9}}$$

[when resistor value is in Ω , capacitor is in F then frequency is in Hz.
 $10k\Omega = 10 \times 10^3 \Omega$, $100nF = 100 \times 10^{-9} F$

$$= 159 \text{ Hz}$$

Problem 3: A signal contains frequencies 200Hz, 300Hz, 700Hz and 1kHz. Design an appropriate filter which will pass 700Hz with ~~an~~ amplification ~~of 10~~ of 2.

Solⁿ: As the filter ~~blocks~~ ^{allows} some middle frequency we need to use a bandpass filter to do this.

Let, first consider the low pass filter. The cut-off frequency will be 700Hz or higher than 700Hz.

Assume, $f_c = 750 \text{ Hz}$ [this must be lower than the next unallowed frequency]

$$\text{So, } \frac{1}{2\pi R_1 C_1} = 750$$

$$\text{Let, } R_1 = 1 \text{ k}\Omega$$

$$\text{Then, } C_1 = \frac{1}{2 \times 3.1416 \times 1 \times 10^3 \times 750} = 0.212 \mu\text{F}$$


Now, Assume $f_c = 500 \text{ Hz}$ for high pass filter:

$$\text{So, again } \frac{1}{2\pi R_2 C_2} = 500$$

$$\text{Let } R_2 = 10 \text{ k}\Omega.$$

$$\text{Then } C_2 = \frac{1}{2 \times 3.1416 \times 1 \times 10^4 \times 500} = 0.318 \text{ nF}$$

The circuit:

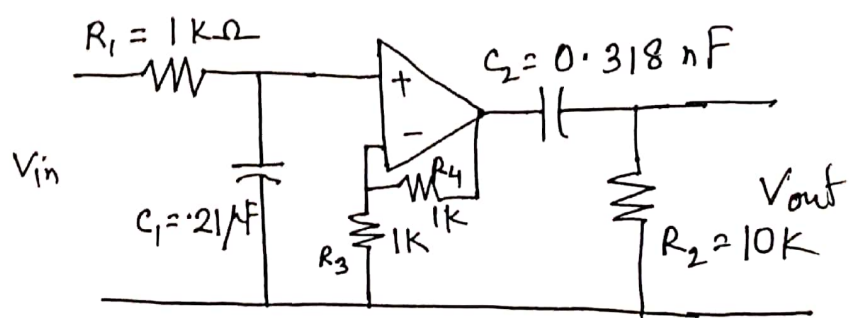

Gain is given as 2:

$$\text{Let, } R_3 = 1 \text{ k}$$

$$\text{So, } 1 + \frac{R_4}{R_3} = 2$$

$$\Rightarrow R_4 = 1 \text{ k}$$